


# STATCOM

## EMERGING FACTS CONTROLLERS


❖ SVC

❖ STATCOM


# SVC

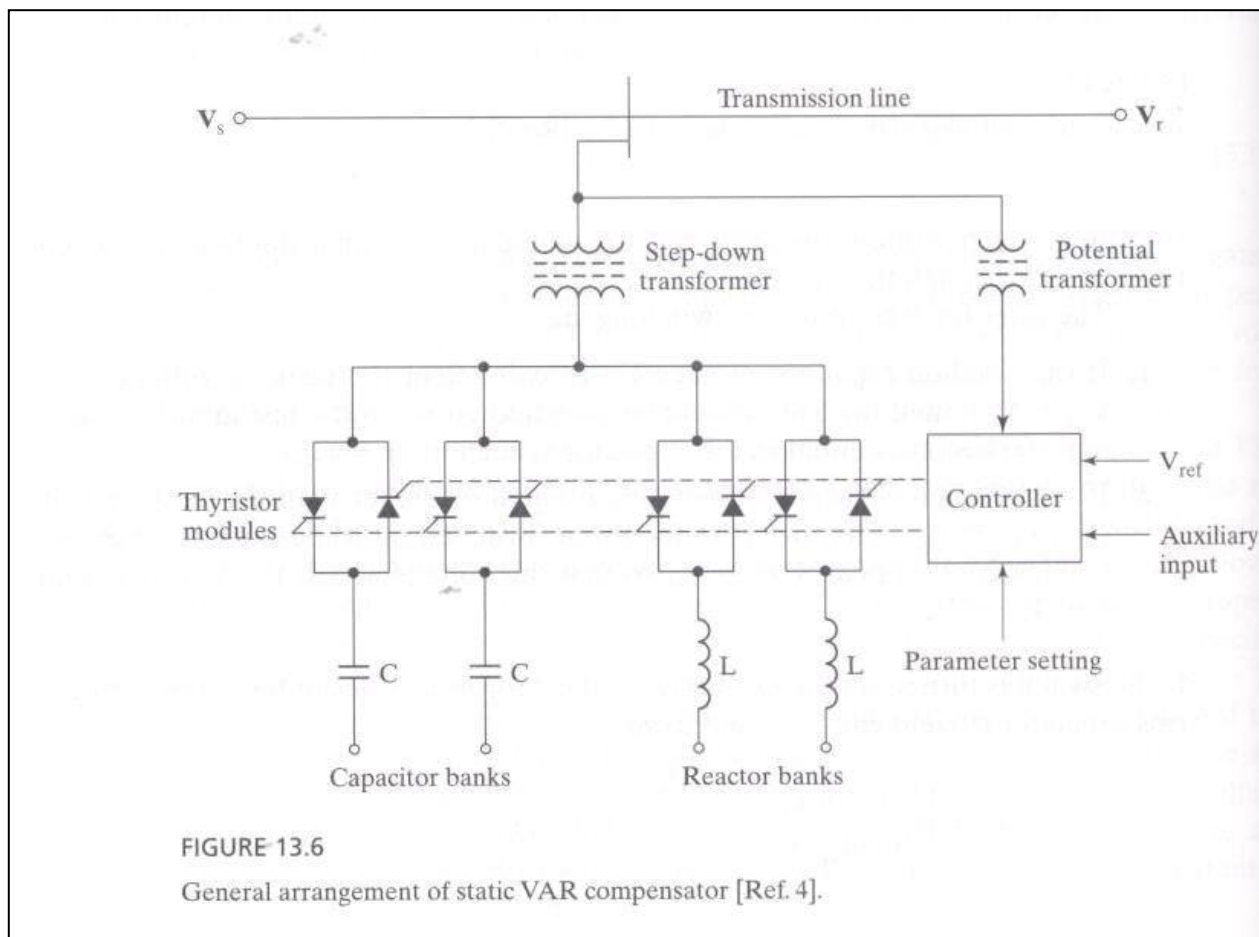

# TCSC CONTROLLER

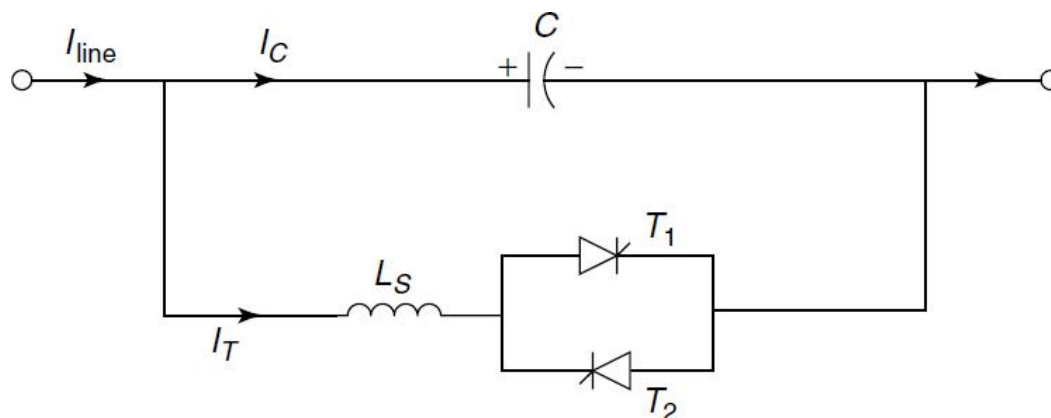

A basic TCSC module

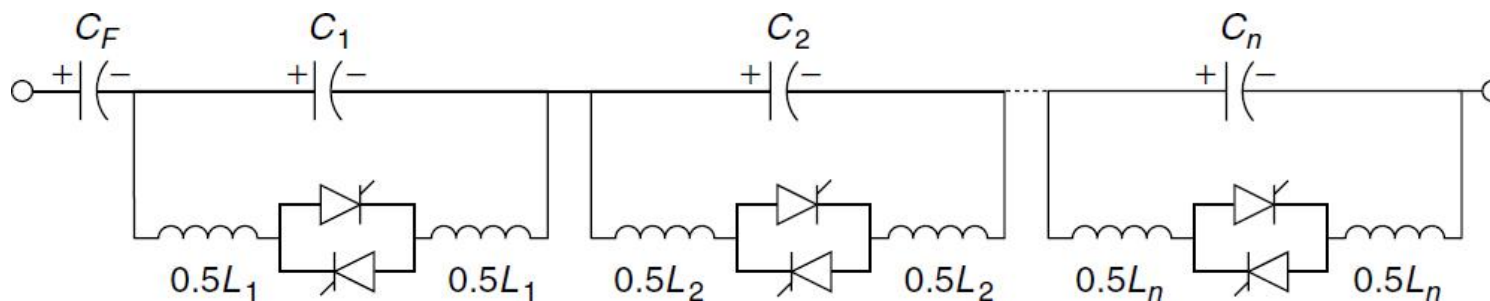

A typical TCSC system.

# STATCOM - Static Synchronous Compensator

It is a solid-state switching converter, **capable of generating or absorbing independently controllable real and reactive power** at its output terminals when it is fed from an **energy source**.

STATCOM is considered as **voltage-source converter** that, from a given input of dc voltage, produces a set of 3-phase ac-output voltages, each in phase with and coupled to the corresponding ac system voltage through a relatively small reactance

## STATCOM can improves


1. the dynamic voltage control in transmission and distribution systems;
2. the power-oscillation damping in power-transmission systems;
3. the transient stability;
4. the voltage flicker control; and
5. the control of not only reactive power but also (if needed) active power in the connected line, requiring a dc energy source.

## STATCOM structure

1. it occupies a small footprint,
2. it factory-built equipment, thereby reducing site work and commissioning time;
3. it uses encapsulated electronic converters, thereby minimizing its environmental impact.

A STATCOM is similar to an ideal synchronous machine, which generates a balanced set of three sinusoidal voltages—at the fundamental frequency—with controllable amplitude and phase angle.


# STATCOM power circuit

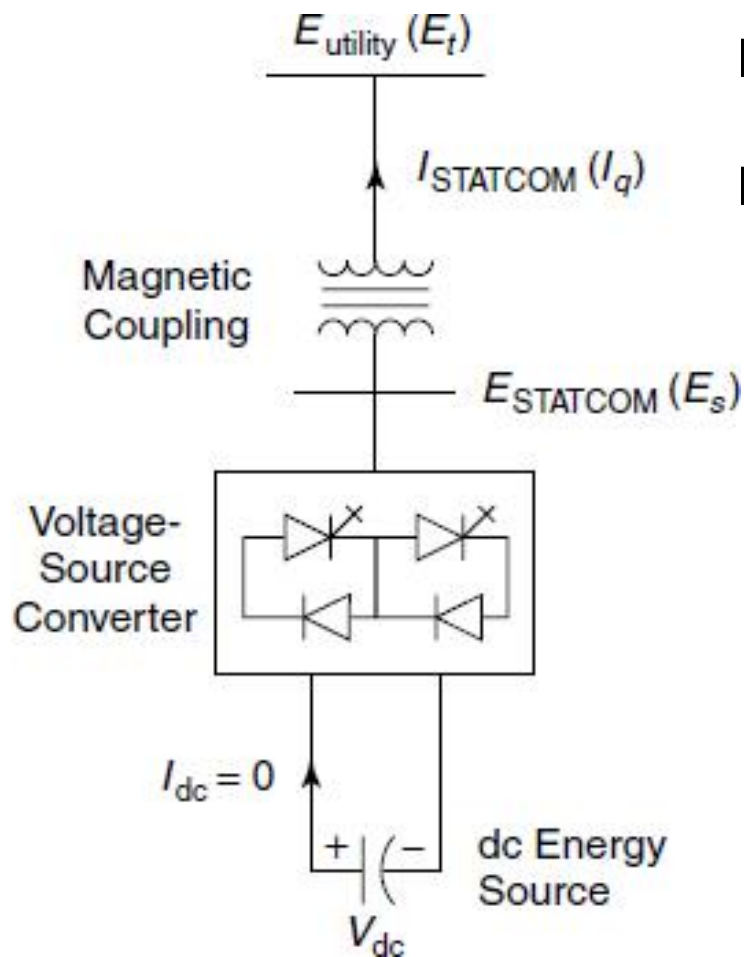
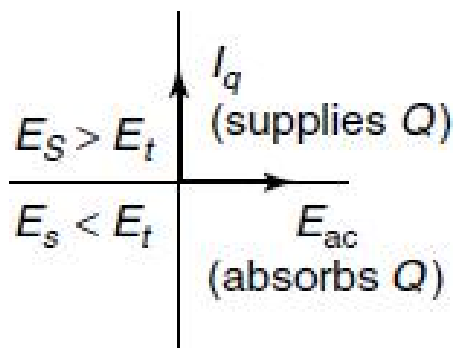
## Reactive Power Generation

Magnitude  $E_s > E_t \rightarrow$  Generates reactive power

Magnitude  $E_s < E_t \rightarrow$  Absorbs reactive power



## When supplying/absorbing Reactive Power

If the amplitude of the **output voltage is increased above that of the utility bus voltage**,  $E_t$ , then a current flows through the reactance from the converter to the ac system and the converter **generates capacitive-reactive** power for the ac system.

If the **amplitude of the output voltage is decreased below the utility bus voltage**, then the current flows from the ac system to the converter and the converter **absorbs inductive-reactive power from the ac system**.

If the output voltage equals the ac system voltage, the **reactive-power exchange becomes zero**, in which case the STATCOM is said to be in a **floating state**.




In reactive power generation, the real power provided by the dc source as input to the converter must be **zero**. The primary need for the capacitor is to provide a **circulating-current path** as well as a voltage source.

In practice, the semiconductor switches of the converter are not lossless, **so the energy stored in the dc capacitor is eventually used to meet the internal losses** of the converter, and the dc capacitor voltage diminishes.

Hence by making the output voltages of the converter **lag behind the ac-system voltages by a small angle** (usually in the 0.1–0.2 degree range), the converter absorbs a small amount of real power from the ac system to **meet its internal losses** and keep the capacitor voltage at the desired level.

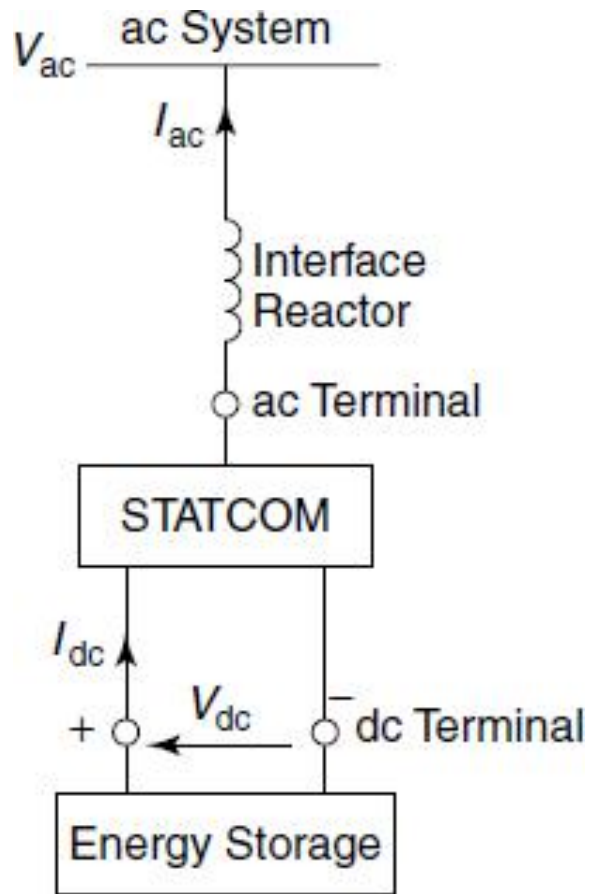
# STATCOM power circuit with energy storage


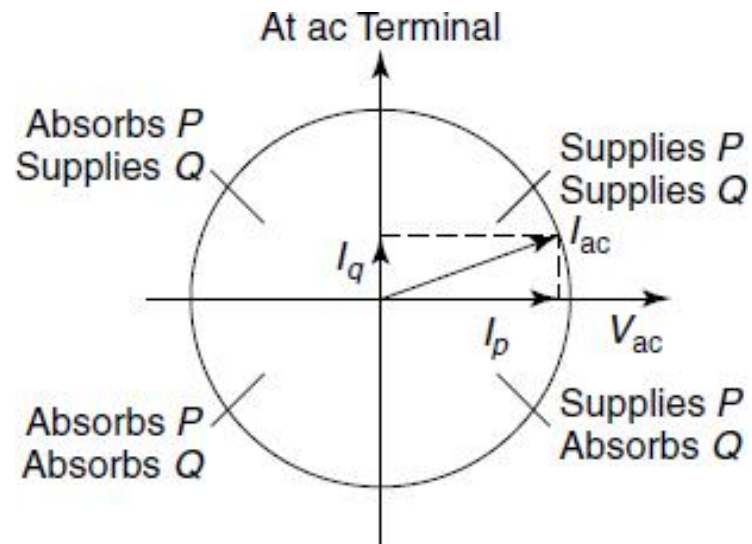
## Real Power Generation

Phase  $E_s$  leads  $E_t \rightarrow$  Generates real power

Phase  $E_s$  lags  $E_t \rightarrow$  Absorbs real power




## When supplying/absorbing Real Power

Adjusting the phase shift between the converter-output voltage and the ac system voltage can similarly control real-power exchange between the converter and the ac system.

If the converter-output voltage is made to **lead** the ac-system voltage, then the converter can **supply real power** to the ac system from its dc energy storage.

If its voltage **lags** behind the ac-system voltage, then the it **absorb** real power from the ac system for the dc system

## V-I Characteristic

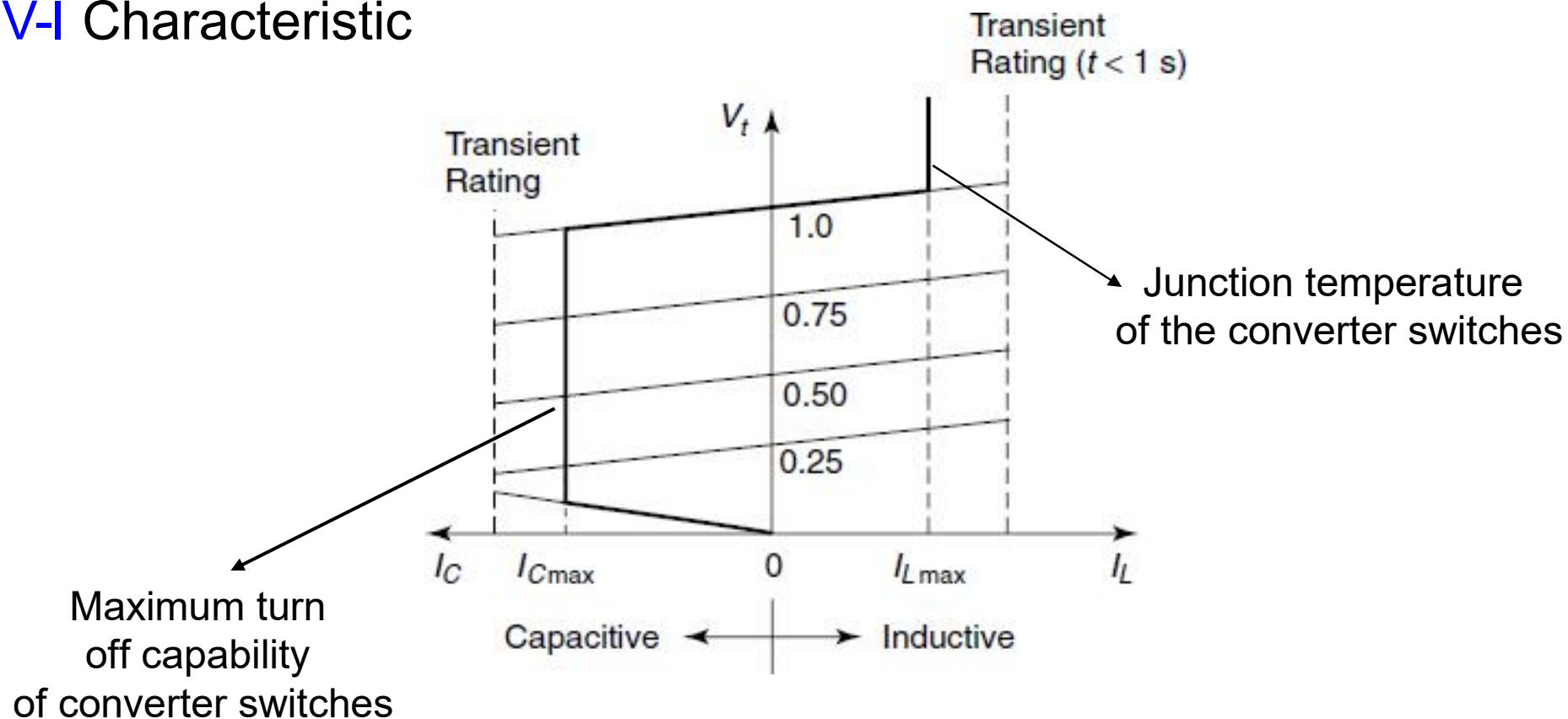

STATCOM can supply both the capacitive and the inductive compensation and is able to independently control its output current over the rated maximum capacitive or inductive range irrespective of the amount of ac-system voltage.

That is, the STATCOM can provide full capacitive-reactive power at any system voltage—even as low as 0.15 pu.

The characteristic of a STATCOM reveals another strength of this technology:

- ❑ It is capable of yielding the full output of capacitive generation almost independently of the system voltage.
- ❑ Hence it supports the system voltage during and after faults where voltage collapse would otherwise be a limiting factor.

The maximum attainable transient overcurrent in the **capacitive region** is determined by the **maximum current turn-off capability** of the converter switches. In the **inductive region**, the **converter switches are naturally commutate**.